

## ASSIGNMENT 9

Uttakarshika

December 16, 2020


- 1 All logic gates shown in the figure have a propagation delay for 20ns. Let  $A=C=0$  and  $B=1$  until time  $t=0$ . At  $t=0$ , all inputs flip(i.e.,  $A=C=1$  and  $B=0$ ) and remain in that state. for  $t$  greater than 0, output  $Z=1$  for a duration of(in ns)-

**SOLUTION-**

Using the graphs and table provided, we come to the conclusion that-

**Z=1 FOR  $t=20\text{ns}-60\text{ns}$**

 **BOOLEAN EXPRESSION  $\overline{A}\overline{B} + A\overline{B}\overline{C}$**



time(t)	A	B	C	B'	X	Z
less than 0	0	1	0	0	0	0
0	1	0	1	0	0	0
20	1	0	1	1	0	1
40	1	0	1	1	1	1
60	1	0	1	1	1	0
80	1	0	1	1	1	0

KEY FOR GRAPHS-  
 ALONG X-AXIS- 1 UNIT=20ns  
 Y-AXIS- 1 UNIT=1

